
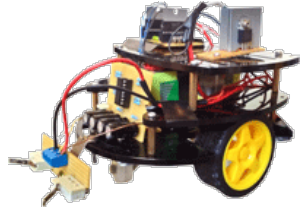


# Monostable multivibrator II

## State machine and signals

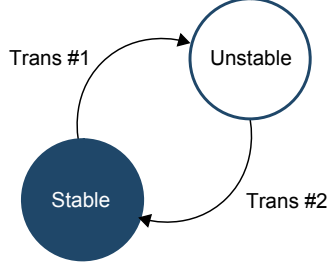


Monostable state machine:





- Trans #1 dependencies:**  
1) MS2, MS4 micro switch sensor, fast discharging of capacitors: C1, C2 & C3, C4 respectively.
- Trans #2 dependencies:**  
1) MS1, MS3 micro switch sensor, fast charging of capacitors: C1, C2 & C3, C4 respectively.  
2) P1, P2, P3, P4, C1, C2, C3 & C4 values.

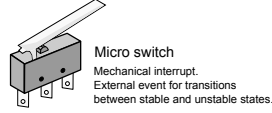Note: Comparator is actually 1bit analog to digital converter.  
Monostable multivibrator schematic could be modified for another sort of analog sensors, like IR sensor for example for fixed charging direction, discharging direction and MS1 and MS3 micro switches.



Signals:

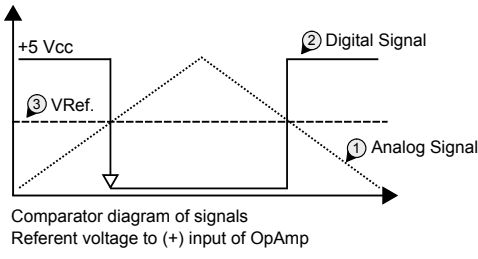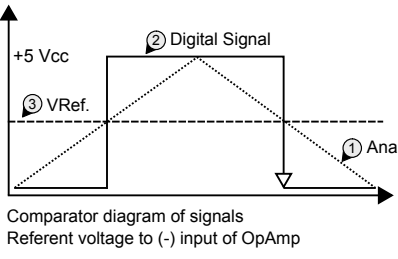


① Analog signal equation:

$$V_c = V_{cc} (1 - e^{-t/RC})$$

$V_c$  - capacitor voltage  
 $V_{cc}$  - power supply voltage  
 $t$  - elapsed time  
 $RC$  - time constant of the RC charging circuit

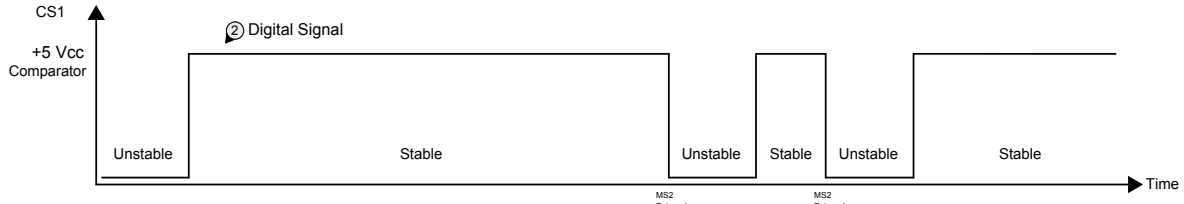Note:  
For simplicity, the analog signal is represented as a linear function.



BA6222 H-Bridge:

F Input / output truth table

5pin (IN)	6pin (IN)	2pin (OUT)	10pin (OUT)
L	L	OPEN	OPEN
L	H	H	L
L	H	L	H
H	H	L	L

Note: HIGH level input is 3.0 V or more  
LOW level input is 1.0 V or less

