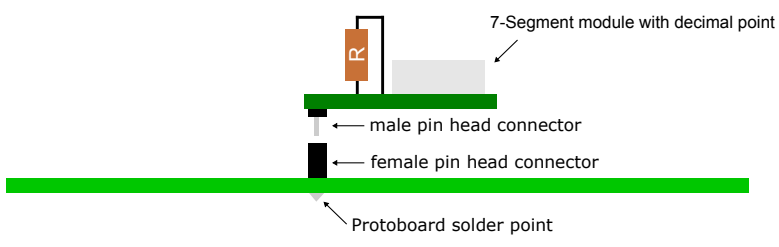


### 7 - Segment display with decimal point

- Eight LEDs in one array.
- 7-Segment display connected to ULN2803 IC outputs.
- Ra - Rh resistor values depends on:
  - maximum allowed LED current and
  - desired intensity of emitted light.
- Light intensity can be controlled with PWM signal.
- ca - common anode.



**Remarks:** Before using, be sure to consult the manufacturer's specifications of integrated circuits ULN2xxx / BA12xxx.

MCU - microcontroller unit.